



Looking inside a torch


A torch uses batteries and a light bulb.

Anything that joins electrical parts, such as batteries and bulbs, is called a circuit.

This is a torch. When you take it apart you find lots of things hidden inside the case.


All the things are joined to make a circuit. Make sure you can see each part.

What you might find inside a torch.

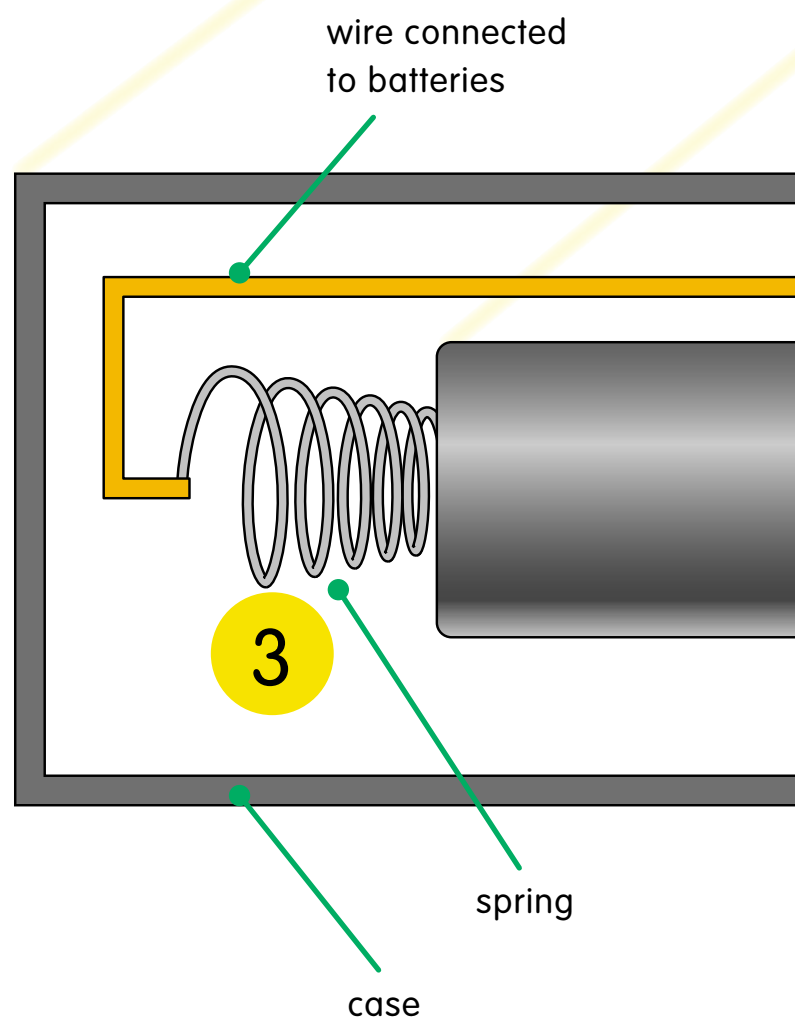

- 1 There is a bulb, which gives out light.
- 2 There are two batteries.
- 3 There are some springs and holders.
- 4 There is a switch for turning the torch on and off.

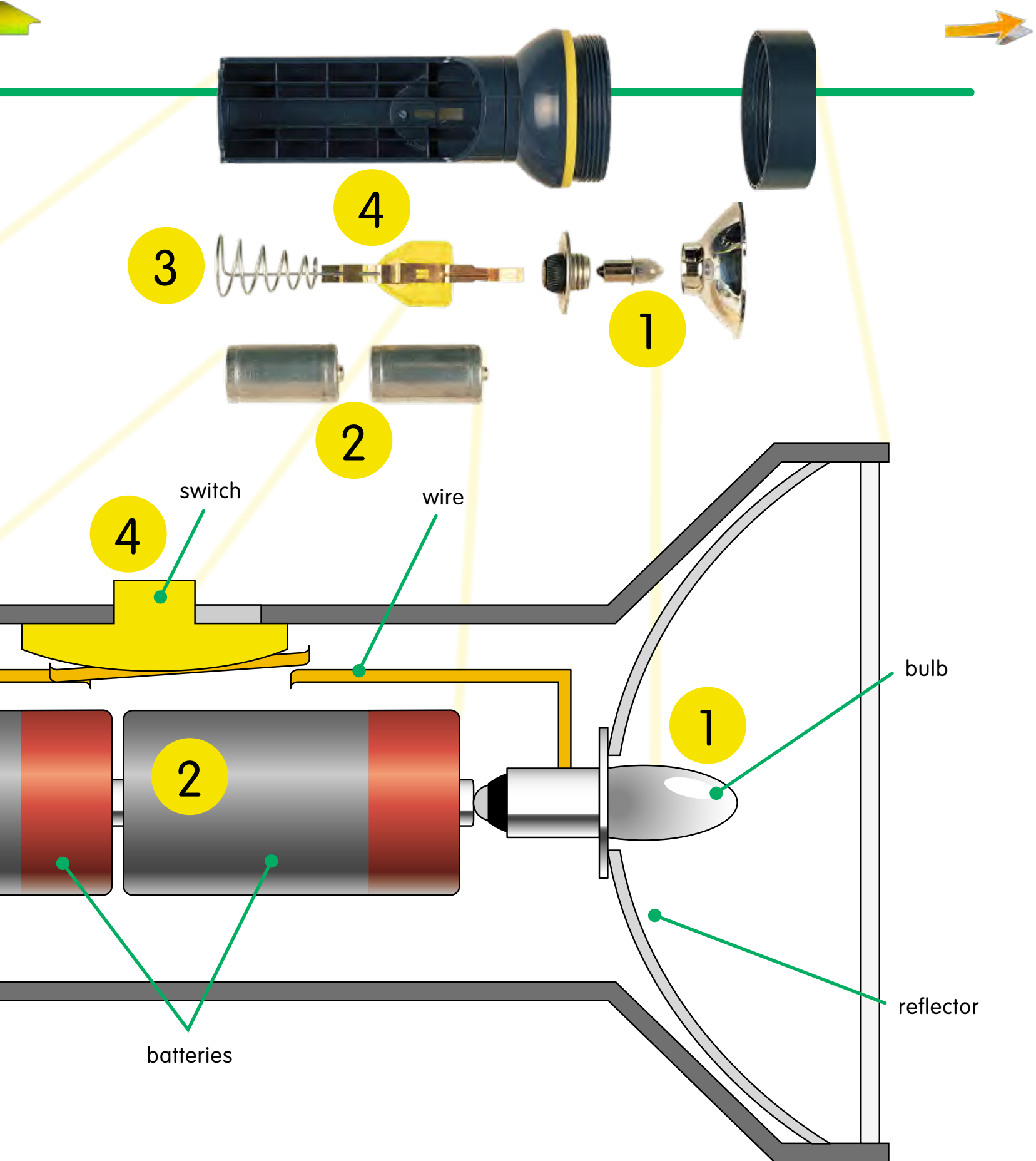Can you take a torch apart and put it back together so that it still works?



You can find out how the torch works on the next page.