




Name: ..... Form: .....

Based on pages 8 and 9 of *Simple electricity*

# Will it light?

Try this...

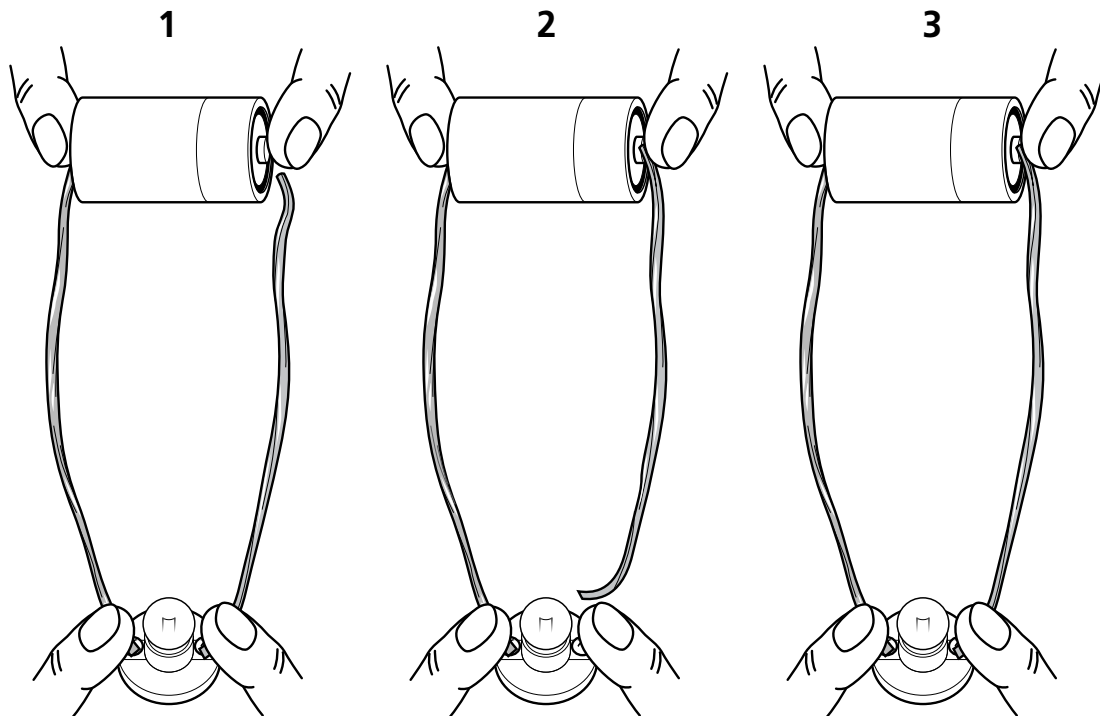1. Look at these four circuits using bulbs, batteries and wires.



2. In the table below put a tick in the prediction column if you think the bulb will light and cross if you think that it will not.

Circuit	Prediction	Test result
1		
2		
3		

3. Test each circuit, and fill in the last column of the table. Put a tick if the bulb lit and a cross if it did not.

**Looking at the results.**

4. How good were your predictions?



.....