



Name: Form:

Based on pages 10 and 11 of *Simple electricity*

My circuit board

Try this...


1. Draw an arrangement of aluminium strips that you would like to make into a circuit board.

2. Mark where you would put the battery and the bulb.

3. Make your circuit board.

4. Test your circuit with the battery and the bulb.

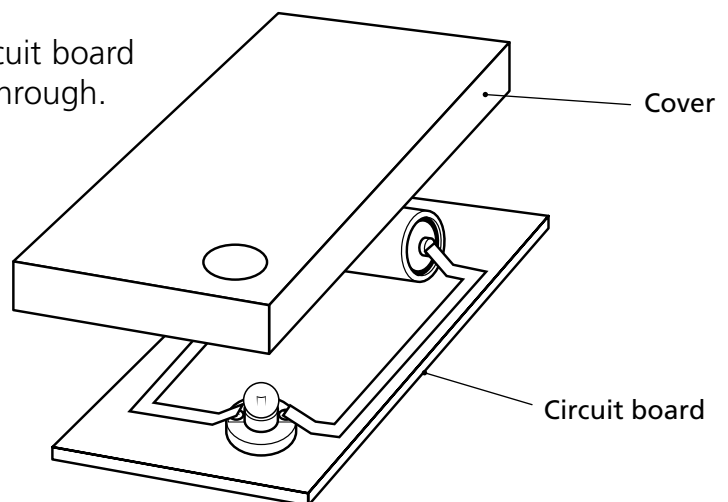5. Make a cardboard cover for your circuit board with a hole in it so the bulb can shine through.



6. When you have finished, disconnect the battery. Keep your circuit board. You will add a switch to it later.