




Name: ..... Form: .....

See pages 8 and 9 of *Simple electricity*

# Making a bulb light

To make a bulb light, you simply need to join the end of the bulb to each end of a battery.

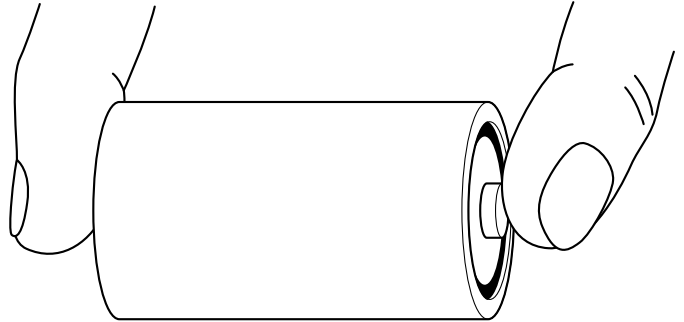**Q1.** (i) Draw on this diagram the things you would use to make the bulb light.  
(ii) Label the things you have drawn.



**Q2.** What is the name for materials that let electricity pass through them?

.....

**Q3.** Give an example of a material that lets electricity pass through it.

.....

**Q4.** What is the name for materials that do not let electricity pass through them?

.....

**Q5.** Give an example of a material that does not let electricity pass through it.

.....

**Q6.** What is the name for the loop that lets electricity flow through it?

.....

