




Name: ..... Form: .....

See pages 14 and 15 of *Simple electricity*
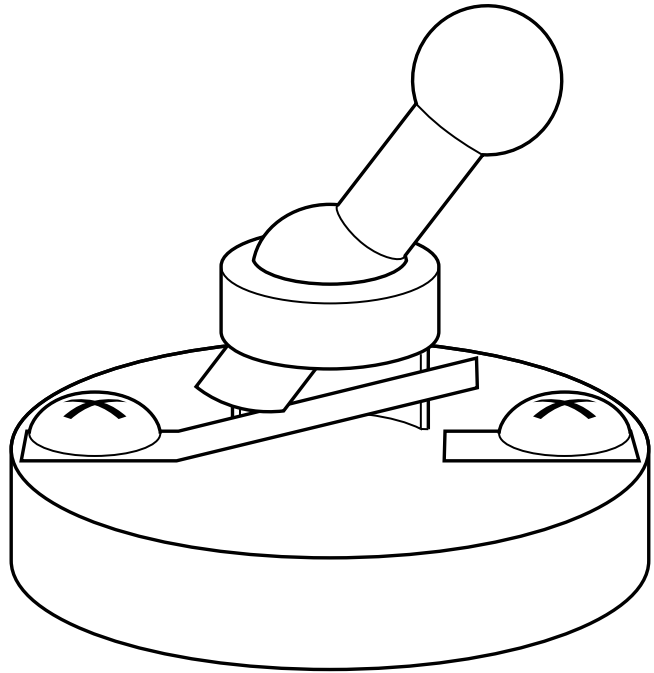
# Switches

Switches are used to break the circuit and control the flow of electricity.



**Q1.** Is the switch on or off?

.....

**Q2.** Explain your answer to question 1.

.....

.....

**Q3.** Will the switch be on or off when the handle is turned the other way?

.....

**Q4.** Explain your answer to question 3.

.....

.....

**Q5.** What are the spring metal plates in a switch called?

.....

**Q6.** What are the ends of a battery called?

.....