




Name: ..... Form: .....

See pages 16 and 17 of *Simple electricity*
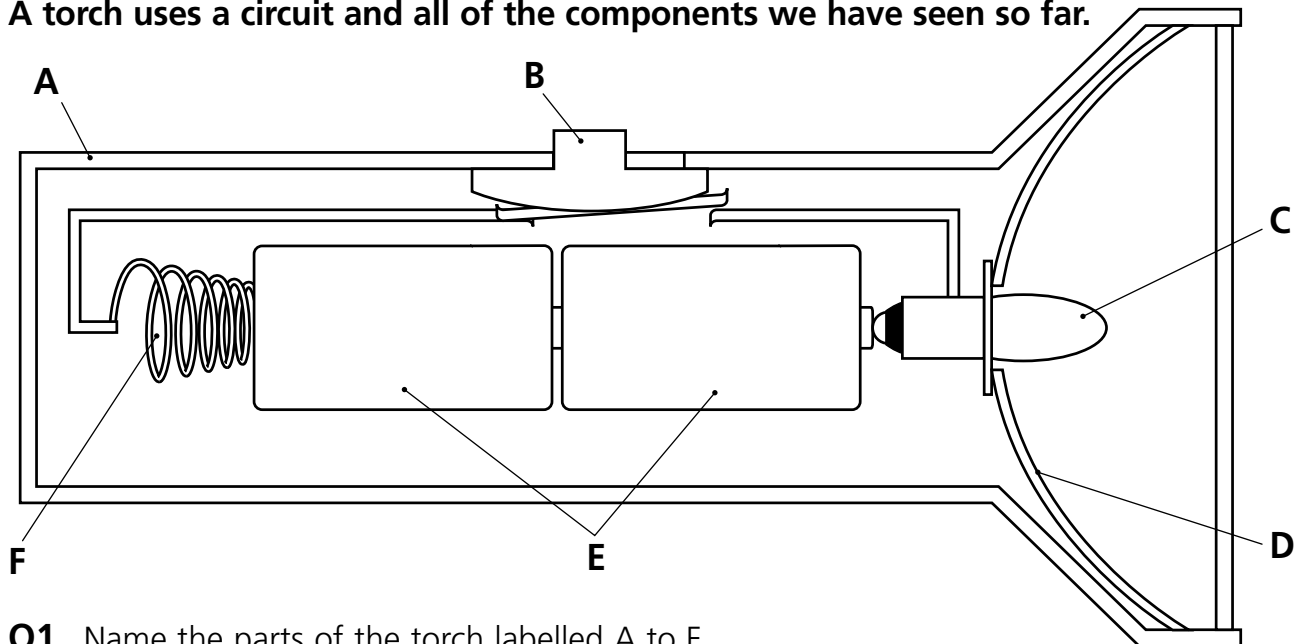
# How a torch works

A torch uses a circuit and all of the components we have seen so far.



**Q1.** Name the parts of the torch labelled A to F.

A ..... B ..... C .....

.

D ..... E ..... F .....

**Q2.** Which part makes the torch easy to carry?



.....

**Q3.** Which part controls the flow of electricity?



.....

**Q4.** Which part provides the electricity?



.....

**Q5.** Which part makes the light?



.....

**Q6.** Name two things that part F does.

1

.....

.

2

.....