



Name: Form:

See pages 20 and 21 of *Simple electricity*

Adding to the loop

You can have as many bulbs in a circuit as you like. You just need to match them to the batteries.

Q1. In the space above, draw a circuit with a switch, four wires, two batteries and two bulbs.

Q2. What kind of circuit have you drawn?



Q3. When you switch on the circuit does (a) the bulb nearest the switch shine brighter than the other; (b) the bulb nearest the switch shine more dimly than the other; or (c) do both bulbs shine with the same brightness?



Q4. If you took one bulb out of the circuit and switched the circuit on again, would the single bulb shine (a) the same as before; (b) brighter than before; or (c) more dimly than before?



Q5. If a third bulb was added, how would they shine compared to two bulbs?



Q6. What voltage do four 1.5V batteries give?

