



Name: ..... Form: .....

Based on pages 12 and 13 of *Changing circuits*

# Series and parallel circuits

Try this...

1. Set up the circuit as shown in Diagram 1 and switch it on.

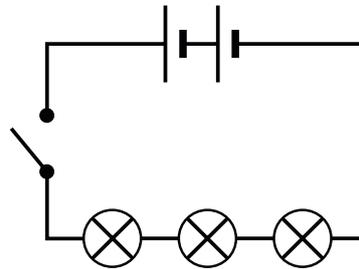


Diagram 1

2. How brightly or dimly do the bulbs shine?

.....

3. Set up the circuit as shown in Diagram 2 and switch it on.

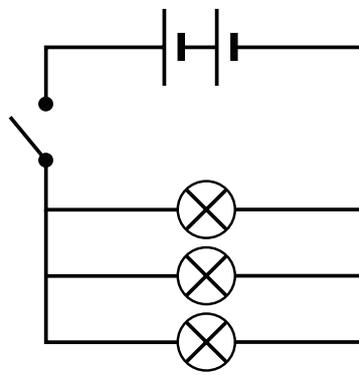


Diagram 2

4. How brightly or dimly do the bulbs shine?

.....

5. Draw a diagram of a parallel circuit with a bulb and a buzzer in it. Check it with your teacher.



6. If your teacher approves, make the circuit and switch it on.

7. What do you find?

.....

8. Predict what will happen if you add another bulb in parallel with the buzzer and the first bulb.

.....

9. Test your prediction. What do you find?

.....