



Name: Form:

See pages 20 and 21 of *Changing circuits*

Home circuits

Your home electricity supply makes use of the circuits and fuses shown on the previous pages.


Q1. Name the parts labelled B, D, E and F.

B

D

E

F

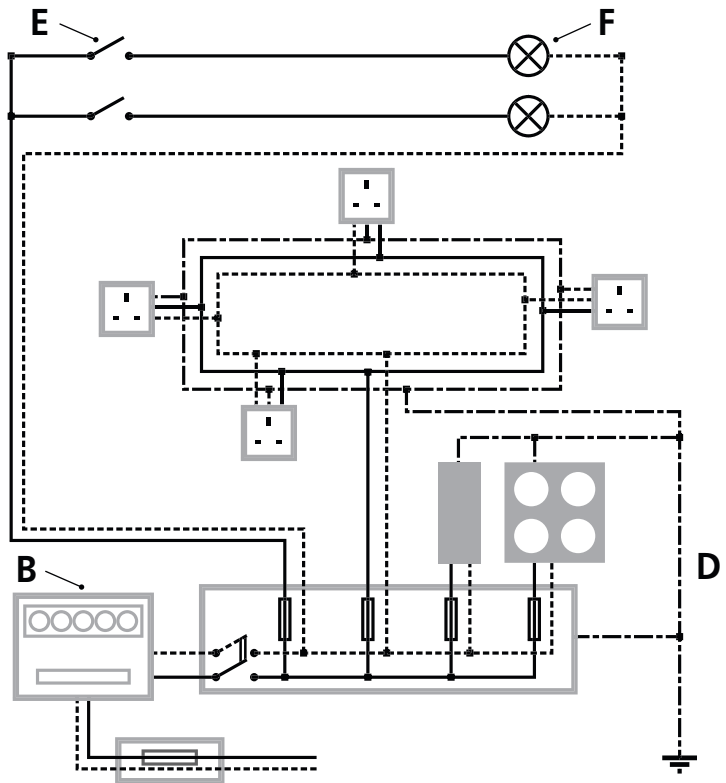

Q2. What carries electricity along the street?

.....

Q3. (i) What is the first thing that electricity passes through when it enters a home?

.....

(ii) Label this device with an A on the diagram.

(iii) How does this device protect the home?

.....

Q4. What does device B do?

.....

.....

Q5. What is the name of the wire that brings electricity to an appliance?

.....

Q6. What kind of circuit is used for the sockets in the home?

.....