

## CurriculumVisions Lesson

Students: fill in next to the word answer and return the document for assessment.

### Science

Book: Simple electricity (4F)

Pages 10-17

Everything here is based on our Curriculum Visions book Simple electricity (4F)

In this segment, we are going to learn about how to make circuits.

#### Part 1

You will need to go to pages 10-11 of the book. If your teacher agrees, use the materials in picture 2 to make a circuit that will light a bulb.

Answer.....

#### Part 2

Go to pages 12-13. How can you know how many batteries to use with a bulb?

Answer.....

How many 1.5 volt batteries do you need to use to light up a 3-volt battery?

Answer.....

#### Part 3

Go to pages 14-15

What does a switch do?

Answer.....

If your teacher agrees, add a switch to your circuit.

Answer.....

Part 4

Go to pages 16-17

How is a torch different from the circuit that you made?

Answer.....

-----

If you are interested in this topic continue to browse the book and watch our amazing videos. They start right on the book cover.